

ETE Transistor

Samuel Nösslböck

April 2022


1 Introduction

The known variables are

$$U_0 = 96V, \quad R_L = 13.2\Omega, \quad L = 60mH, \quad f_T = 1.5, 6, 24, 96KHz, \quad t_{TURN} = 12\mu s, \quad \frac{T_{OFF}}{T_{ON}} = 1.5 \quad (1)$$

2 PWM Signal

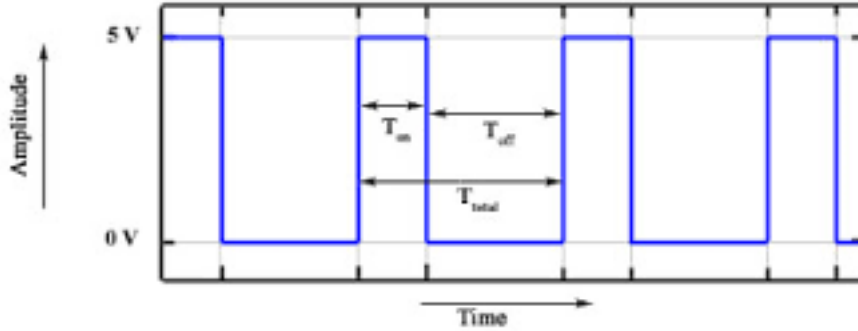The bare PWM Signal has a Voltage over time graph depending on the frequency f_T and the relation between active and inactive current flow.



The total time T_{total} is calculated as follows

$$T_{total} = T_{ON} + T_{OFF} = \frac{1}{f_T} = \underline{666\mu s, 166\mu s, 41.6\mu s, 10.4\mu s} \quad (2)$$

$$T_{ON} = \frac{T_{total}}{2.5} \quad T_{OFF} = T_{total} - T_{ON} \quad (3)$$

So the the variables for the four different frequencies result in

f_T	T_{total}	T_{ON}	T_{OFF}
1.5	666 μs	266	400
6	166 μs	66.6	100
24	41.6 μs	16.7	25
96	10.4 μs	4.17	6.25

3 Turn-Off sequence approximations


As the circuit has a given magnetism, the curves of voltage $u(t)$ and $i(t)$ are not vertical

$$u_{OFF}(t) = \frac{U_0}{2 \cdot t_P} \cdot t \cdot e^{-\frac{t}{2 \cdot t_P}} + U_0 \cdot (1 - e^{-\frac{t}{T_{OFF}}}); \quad t_P = \frac{T_{OFF}}{2} \quad (4)$$




For the approximation of the current, the sigmoid function is used
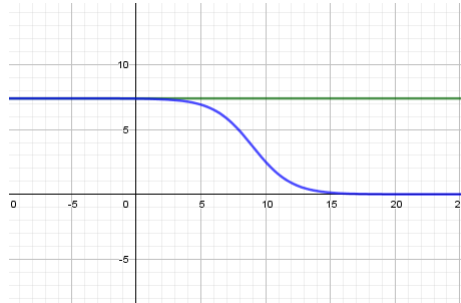
$$i_{OFF}(t) = \frac{I_0}{1 + e^{\frac{x \ln(I_0)}{t_P/2}}} \quad t_P = \frac{T_{OFF}}{2} \quad (5)$$



So the power is calculated using
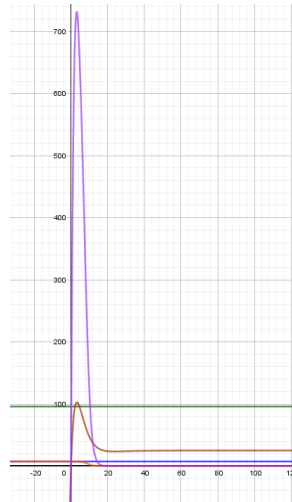
$$p_{OFF}(t) = i_{OFF}(t) \cdot u_{OFF}(t) \quad (6)$$



4 Calculation

The actual calculation of the average power-usage is calculated as follows

$$I_0 = \frac{U_0}{R_L} = \underline{7.27A} \quad P_0 = I_0 \cdot 1V = \underline{7.27W} \quad (7)$$

$$\overline{P_{CE}} = \frac{P_0 \cdot \Delta T_{OFF} + \overline{P_{OFF}} \cdot T_{TURN}}{\Delta t_{ON} + \Delta t_{OFF}}; \quad \overline{P_{OFF}} = \frac{1}{T_{TURN}} \cdot \int_0^{T_{TURN}} p_{OFF}(t) dt \quad (8)$$

So the average power consumption for the four given frequencies

f_T	$\overline{P_{OFF}}$	$\overline{P_{CE}}$
1.5	400W	11.6W
6	400W	33.1W
24	400W	199.27W
96	400W	465.9W

The last result does barley make sense, because the total period approaches the turn time

5 Magnetism without diode

Without a diode, the energy of magnetism only passes out slowly. The energy of magnetism is calculated using

$$E_M = \frac{L \cdot I^2}{2} \quad (9)$$

So an approximation would be

$$i(t) = I_0 \cdot e^{\frac{-xR}{L}} \quad (10)$$